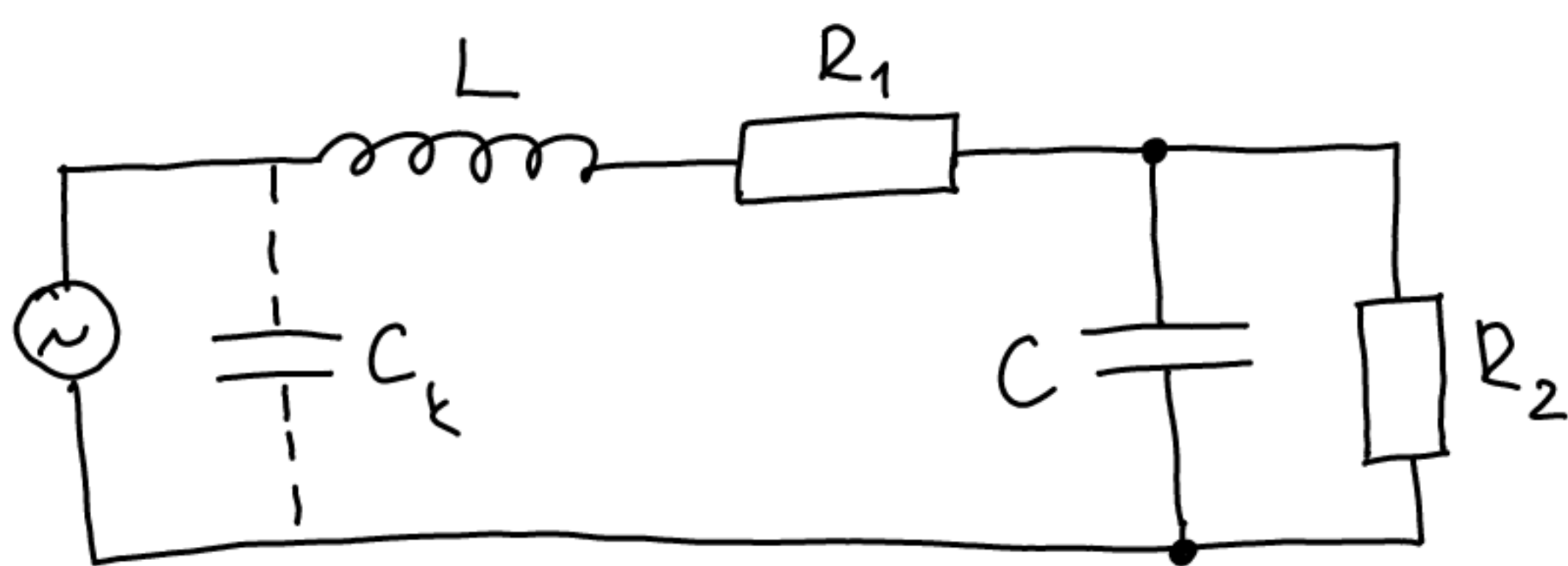




$$R_1 = 500 \, \Omega$$

$$R_2 = 1.5 \, k\Omega = 1500 \, \Omega$$

$$L = 420 \, mH = 0.42 \, H$$

$$C = 210 \, \mu F = 210 \cdot 10^{-9} \, F$$

$$u(t) = 35.35 \cdot \sin(\omega \cdot t + 1.234) \, V$$

a) I.a. $U = \frac{35.35}{\sqrt{2}} \angle 1.234 \, \text{rad} = \boxed{25.00 \angle 70.7^\circ = 8.263 + 23.595j}$

I.b. $f = 500 \, Hz \rightarrow \omega = 2 \cdot \pi \cdot f = \boxed{3142 \, \frac{\text{rad}}{s}}$

I.c. $Z_L = \omega \cdot L \angle 90^\circ = \boxed{1320 \angle 90^\circ \, \Omega = 0 + 1320j}$

$$Z_C = \frac{1}{\omega \cdot C} \angle -90^\circ = \boxed{1516 \angle -90^\circ \, \Omega = 0 - 1516j}$$

II.a. R_1 i L su spojeni **SERIJSKI**

$$Z_1 = R_1 + Z_L = \boxed{500 + 1320j = 1412 \angle 69.3^\circ \, \Omega}$$


II.b. R_2 i C su spojeni **PARALELNO**

$$Z_2 = \frac{R_2 \cdot Z_C}{R_2 + Z_C} = \frac{(1500 \cdot 1516) \angle 0^\circ - 90^\circ}{1500 - 1516j} = \frac{(1500 \cdot 1516) \angle -90^\circ}{2133 \angle -45.3^\circ} =$$

$$Z_2 = 1066 \angle -44.7^\circ \Omega = 757.7 - 749.8 \cdot i$$

II.c. Zato što je to mješoviti spoj i treba ga se svesti na serijski ili paralelni da bi se mogla izračunati ukupna impedancija.

II.d. Spoj Z_1 i Z_2 je SERIJSKI.

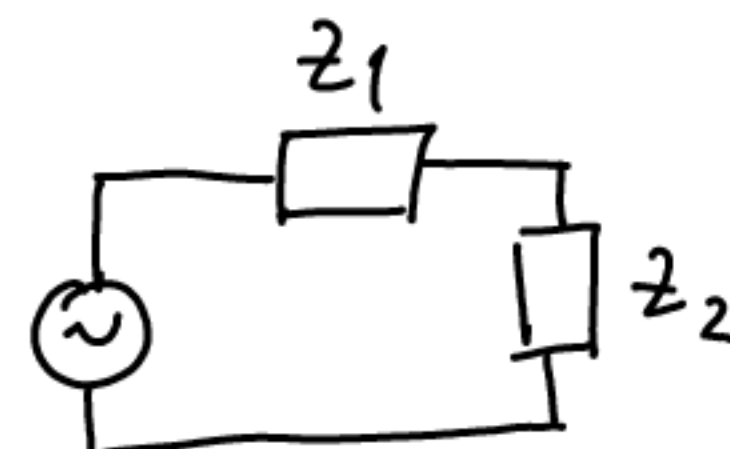

$$Z_{uk} = Z_1 + Z_2 = (500 + 1320i) + (757.7 - 749.8i) =$$

$$= 1257.7 + 570.2i = 1381 \angle 24.4^\circ \Omega$$

III.a. $I_{uk} = \frac{U}{Z_{uk}} = \frac{25 \angle 70.7^\circ}{1381 \angle 24.4^\circ} = 18.10 \angle 46.3^\circ \text{ mA}$

$$i_{uk}(t) = 25.60 \cdot \sin(3142 \cdot t + 0.808) \text{ mA}$$

III.b. Za izračunati I_L i I_{R_2} potreban je napon U_{Z_2} koji je isti u obje grane: $U_{Z_2} = U_{R_2} = U_L$

III.c. Napon se od izvora do čvora "troši" na R_1 i L .

$$U_L = I_{uk} \cdot Z_L = (18.1 \cdot 10^{-3} \cdot 1320) \angle 46.3^\circ + 90^\circ = 23.89 \angle 136.3^\circ \text{ V}$$

$$= 23.89 \angle 136.3^\circ \text{ V} = -17.27 + 16.51i$$

$$U_{R_2} = I_{uk} \cdot R_2 = (18.1 \cdot 10^{-3} \cdot 500) \angle 46.3^\circ + 0^\circ =$$

$$= 9.05 \angle 46.3^\circ \text{ V} = 6.252 + 6.543i$$

III.d. $U_{RC} = U - U_L - U_{R_1} =$

$$= (8.263 + 23.595i) - (-17.27 + 16.51i) - (6.252 + 6.543i) =$$

$$= 19.281 + 0.542i = 19.29 \angle 1.6^\circ \text{ V}$$

III.e.

$$U_{RC} = I_{uk} \cdot Z_2 = (18.1 \cdot 10^{-3} \cdot 1066) \angle 46.3^\circ - 44.7^\circ =$$

$$= 19.29 \angle 1.6^\circ \checkmark$$

III.f. $I_c = \frac{U_{RC}}{Z_c} = \frac{19.29 \angle 1.6^\circ}{1516 \angle -90^\circ} = 12.72 \angle 91.6^\circ \mu\text{A}$

$$I_{R_2} = \frac{U_{RC}}{R_2} = \frac{19.29 \angle 1.6^\circ}{1500 \angle 0^\circ} = 12.86 \angle 1.6^\circ \mu\text{A}$$

IV.a. $S_{uk} = U \cdot I_{uk}^* = 25 \angle 70.7^\circ \cdot 18.1 \cdot 10^{-3} \angle -46.3^\circ =$

$$= 452.5 \angle 24.4^\circ \text{ mVA}$$

kut mora biti isti kao
od Z_{uk} ! (i je)

$$\underline{\text{IV.b.}} \quad S_{uk} = (452.5 \cdot \cos(24.4^\circ) + 452.5 \cdot \sin(24.4^\circ)j) \text{ mVA} =$$

$$= 412.1 + 186.9 \cdot j$$

$$\Rightarrow \boxed{\begin{array}{l} P_{uk} = 412.1 \text{ mW} \\ Q_{uk} = 186.9 \text{ mVAR} \end{array}}$$

$$\underline{\text{IV.c.}} \quad S_{uk} = U \cdot I_{uk}^* = U \cdot \frac{U^*}{Z_{uk}^*} = \frac{|U|^2}{Z_{uk}^*} = \frac{25^2}{1381 \angle -24.4^\circ} = 0.4526 \angle 24.4^\circ$$

$$\underline{\text{IV.d.}} \quad S_{uk} = U \cdot I_{uk}^* = I_{uk} \cdot Z_{uk} \cdot I_{uk}^* = |I|^2 \cdot Z_{uk} =$$

$$= (18.1 \cdot 10^{-3})^2 \cdot 1381 \angle 24.4^\circ =$$

$$= 0.4524 \angle 24.4^\circ$$

↑
tu je jedina
razlika, to je
zbog zaokruživanja
međurezultata

$$\underline{\text{IV.e.}} \quad P_{R_1} = |I_{uk}|^2 \cdot R_1 = 18.1^2 \cdot 500 \cdot 10^{-6} \angle 0^\circ = \boxed{163.8 \text{ mW}}$$

$$P_{R_2} = |I_{uk}|^2 \cdot R_2 = 12.86^2 \cdot 1500 \cdot 10^{-6} \angle 0^\circ = \boxed{248.1 \text{ mW}}$$

provjera: $P_{R_1} + P_{R_2} = 411.9 \approx P_{uk} \quad \checkmark$

$$Q_L = |I_{uk}|^2 \cdot Z_L = 18.1^2 \cdot 1320 \cdot 10^{-6} \angle +90^\circ = \boxed{+432.4 \text{ mVAR}}$$

$$Q_C = |I_c|^2 \cdot Z_C = 12.72^2 \cdot 1516 \cdot 10^{-6} \angle -90^\circ = \boxed{-245.3 \text{ mVAR}}$$

provjera: $Q_L + Q_C = 187.1 \approx Q_{uk} \quad \checkmark$

b) I. Napon će bit isti kao napon izvora, jer je spojen paralelno na izvor.

$$\text{II. } Z_{C_k} = \frac{1}{\omega \cdot C_k} \angle -90^\circ$$

$$\text{III. } Q_{C_k} = U \cdot I_{C_k}^* = \frac{U \cdot U^*}{Z_{C_k}^*} = \frac{|U|^2}{\frac{1}{\omega \cdot C_k} \angle +90^\circ} = \omega \cdot C_k \cdot |U|^2 \angle -90^\circ$$

IV. Zato što je napon prema ostatku strujnog kruga ostao isti, a time i struje i snage.

$$\begin{aligned} \text{V. } S_{uk}' &= S_{uk} + Q_{C_k} = 0.4121 + 0.1869i - 3142 \cdot 25^2 \cdot C_k \cdot i = \\ &= 0.4121 + \underbrace{(0.1869 - 1963750 \cdot C_k)}_{=0} \cdot i \end{aligned}$$

VI.

$$\Rightarrow 1963750 \cdot C_k = 0.1869 \rightarrow C_k = 9.5175 \cdot 10^{-8} \text{ F}$$

$$\Rightarrow \boxed{C_k = 95.175 \text{ nF}}$$

$$\text{VII. } F.S. = \frac{P}{|S|} = \cos(\varphi_s) ; \text{ ako } P = |S| \text{ onda } \underline{\underline{F.S. = 1}}$$

$$\text{VIII. } F.S. = \frac{P}{|S|} = \frac{0.4121}{0.4525} = \boxed{91.1 \%}$$

$$c) \text{ I. } C_k' = C_k - 20\% \cdot C_k = 0.8 \cdot C_k = \boxed{76.14 \text{ nF}}$$

$$\text{II. } Q_{C_k}' = \omega \cdot C_k' \cdot |U|^2 \angle -90^\circ = \boxed{-0.1495 \text{ VAR}}$$

(vidi b) III.)

$$\text{III. } S_{uk}' = S_{uk} + Q_{C_k}' = 0.4121 + 0.1869 \cdot i - 0.1495 \cdot i =$$

$$= 0.4121 + 0.0374 \cdot i = 0.4138 \angle 5.2^\circ \text{ VA}$$

$$F.S.' = \frac{0.4121}{0.4138} = \boxed{99.6 \%}$$

IV. Budući da razlika u iznosu kapaciteta od 20%

uzrokuje smanjenje faktora snage od manje od 0.5%,

čini se da nije prevažan egzaktni iznos kompenzirajućeg kondenzatora, dok god je istog reda veličine.

d) I. Imaginarni dio ukupne impedancije mora biti 0.

II. Ukupna impedancija ovisi o frekvenciji izvora, zbog Z_L i Z_C .

$$\text{III. } Z_{uk} = Z_L + Z_{R_1} + \frac{Z_{R_2} \cdot Z_C}{Z_{R_2} + Z_C} = \omega \cdot L \cdot i + R_1 + \frac{R_2 \cdot \left(\frac{-i}{\omega C}\right)}{R_2 - \frac{i}{\omega C}} =$$

$$= R_1 + \omega \cdot L \cdot i + \frac{-i \cdot R_2}{\omega \cdot C} \cdot \frac{\left(R_2 + \frac{i}{\omega \cdot C}\right)}{\left(R_2 - \frac{i}{\omega \cdot C}\right)} =$$

$$= R_1 + \omega \cdot L \cdot i + \frac{\left(\frac{-i \cdot R_2^2}{\omega \cdot C} - \frac{\overset{=-1}{\textcircled{i^2}} R_2}{\omega^2 \cdot C^2}\right)}{\left(R_2^2 + \frac{1}{\omega^2 C^2}\right)} =$$

$$= R_1 + \underbrace{\frac{\left(\frac{R_2}{\omega^2 C^2}\right)}{\left(R_2^2 + \frac{1}{\omega^2 C^2}\right)}}_{\text{Re}} + \omega \cdot L \cdot i - \underbrace{\frac{\left(\frac{R_2^2}{\omega \cdot C}\right)}{\left(R_2^2 + \frac{1}{\omega^2 C^2}\right)} \cdot i}_{\text{Im}}$$

IV. $\text{Im}(Z_{\text{uk}}) = 0 \Rightarrow \omega_{\text{rez}} \cdot L - \frac{\left(\frac{R_2^2}{\omega_{\text{rez}} \cdot C}\right)}{\left(R_2^2 + \frac{1}{\omega_{\text{rez}}^2 C^2}\right)} = 0$

$$\Rightarrow \omega_{\text{rez}} \cdot L = \frac{\left(\frac{R_2^2}{\omega_{\text{rez}} \cdot C}\right)}{\left(R_2^2 + \frac{1}{\omega_{\text{rez}}^2 C^2}\right)} \quad / \cdot \left(R_2^2 + \frac{1}{\omega_{\text{rez}}^2 C^2}\right) \cdot \omega_{\text{rez}} \cdot C$$

$$\Rightarrow \omega_{\text{rez}}^2 \cdot L \cdot C \cdot R_2^2 + \frac{L}{C} = R_2^2$$

$$\Rightarrow \omega_{\text{rez}}^2 = \frac{R_2^2 - \frac{L}{C}}{L \cdot C \cdot R_2^2} = \frac{1}{L \cdot C} - \frac{1}{R_2^2 \cdot C^2}$$

$$\Rightarrow \omega_{\text{rez}} = \sqrt{\frac{1}{L \cdot C} - \frac{1}{R_2^2 \cdot C^2}} = \sqrt{\frac{1}{0.42 \cdot 210 \cdot 10^{-9}} - \frac{1}{1500^2 \cdot 210^2 \cdot 10^{-18}}} =$$

$$= \sqrt{\frac{10 \cdot 10^8}{0.42 \cdot 210} - \frac{10^8}{1.5^2 \cdot 2.1^2}} = 0.11224 \cdot 10^4 \frac{\text{rad}}{\text{s}} =$$

$$= 1122.4 \frac{\text{rad}}{\text{s}}$$

V. $\omega_{\text{rez}} = 2 \cdot \pi \cdot f_{\text{rez}} \Rightarrow f_{\text{rez}} = \frac{\omega_{\text{rez}}}{2 \cdot \pi} = 178.6 \text{ Hz}$

VI. $\omega_{\text{rez}} = \sqrt{\frac{1}{L \cdot C} - \frac{1}{R_2^2 \cdot C^2}} = \sqrt{-0.79365 \cdot 10^4} = \underline{\underline{??!}}$

Frekvencija ne može biti imaginarna! To nema smisla, nije fizičko, ne postoji...

U postupku u IV. dijelili smo jednačinu s ω_{rez} , a to se smije samo ako je $\omega_{\text{rez}} \neq 0$.

Za $\omega = 0$ vidimo da $Z_{\text{uk}} = R_1 + R_2$, dakle isto je $\text{Im}(Z_{\text{uk}}) = 0$. U prijevodu, ne postoji AC napon pri kojem bi takav krug rezonirao.